





SPICE Circuit Schematic & Real Circuit of Audio Frequency Band Detector